

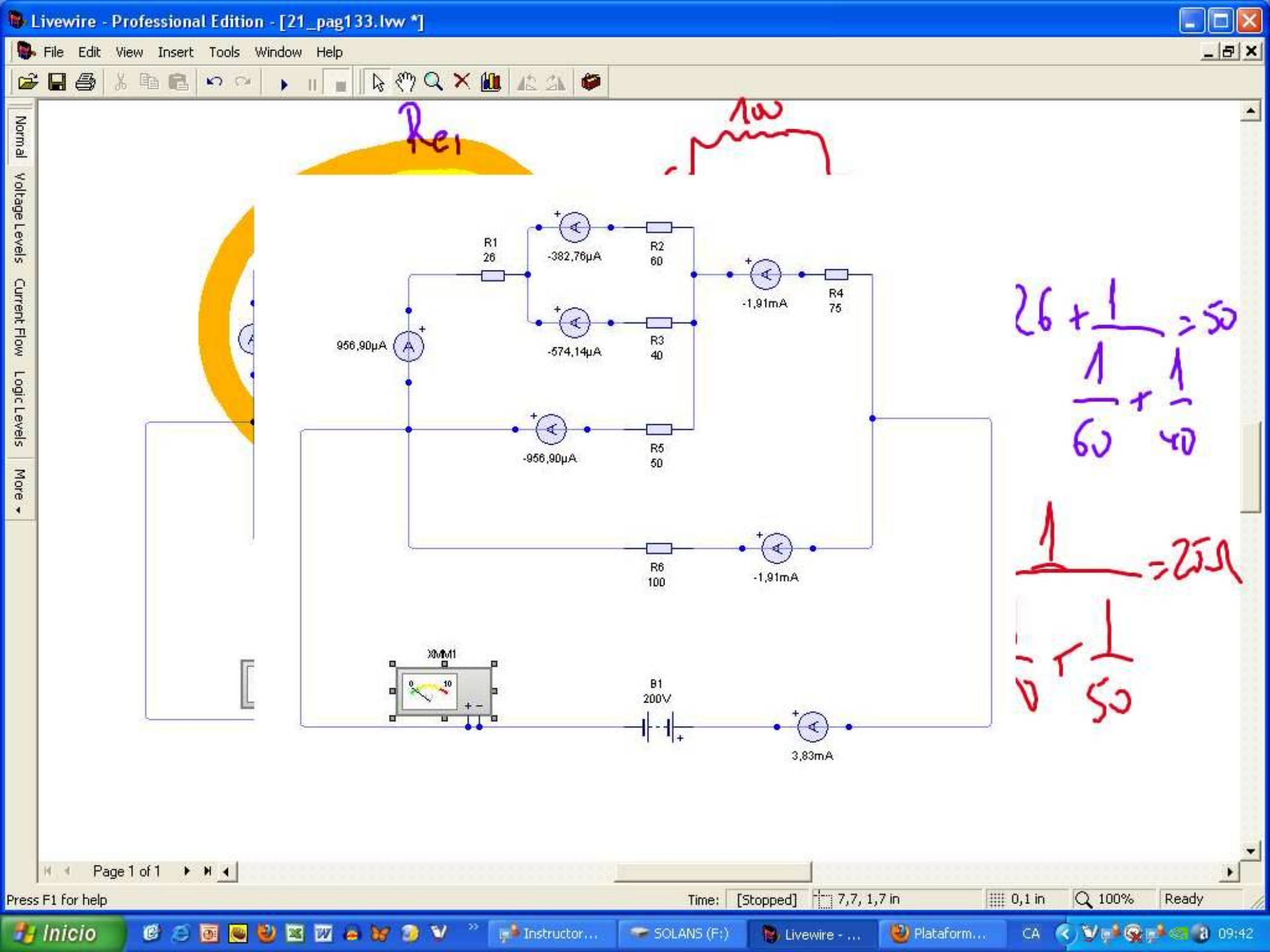



$$R_{e1} = 26 + \frac{1}{\frac{1}{60} + \frac{1}{40}} = 50$$
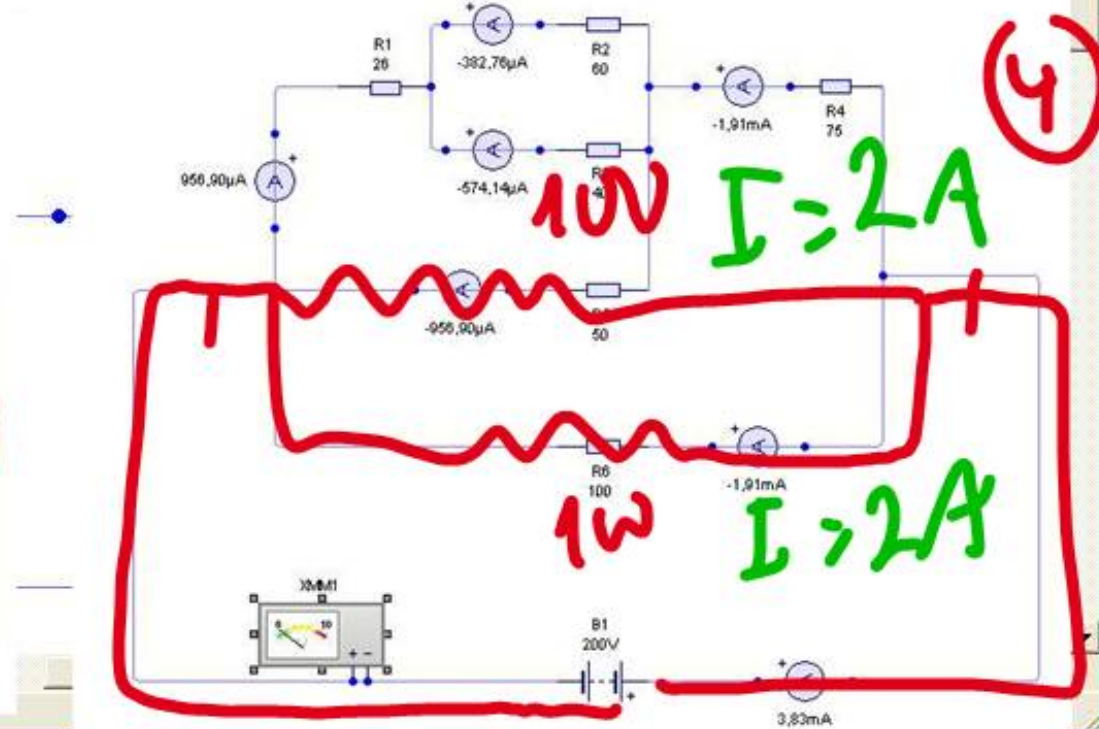
$$R_{e2} = \frac{1}{\frac{1}{50} + \frac{1}{50}} = 25\Omega$$



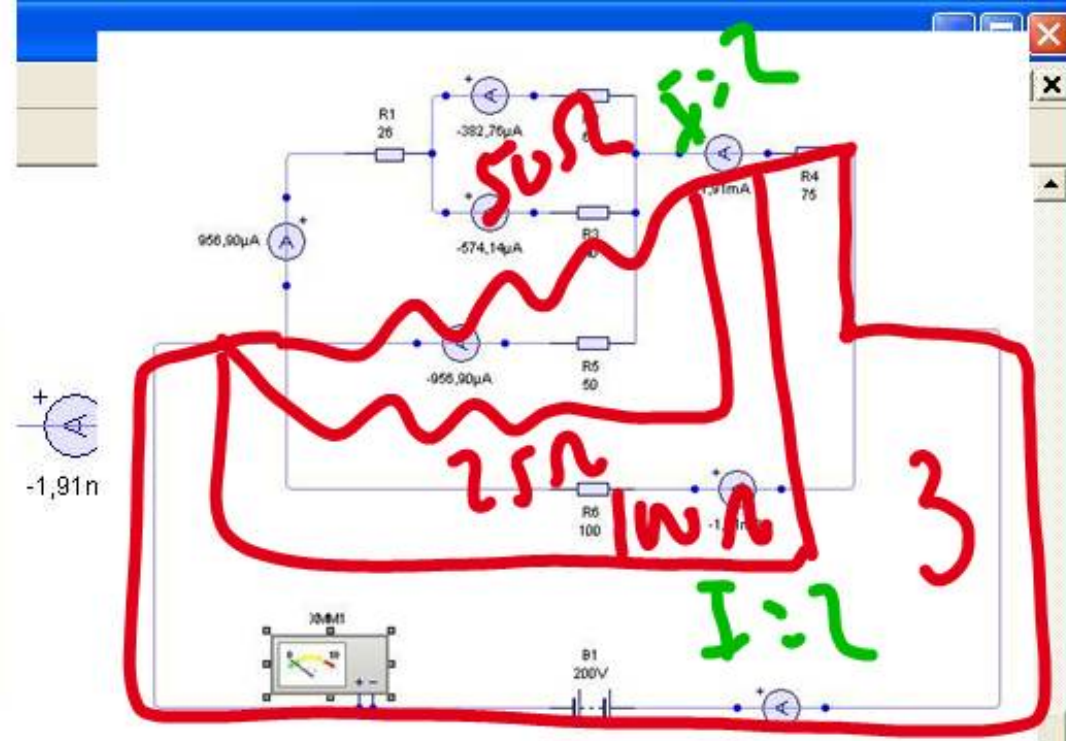



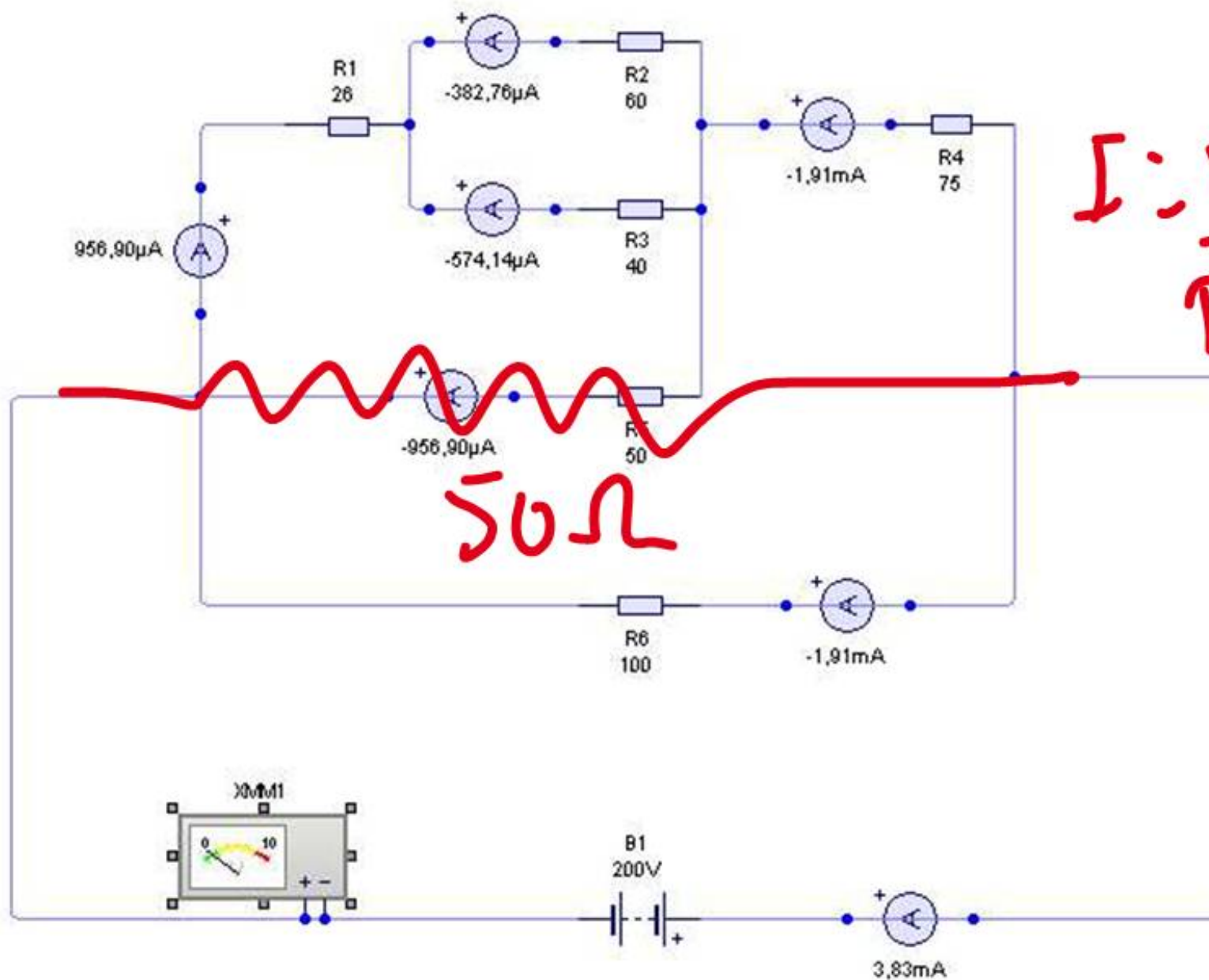

$$I = \frac{V}{R} = 4A$$

50Ω