

# Ohm's Law

- George Simon Ohm (1789-1854) discovered the relationship between:

- VOLTAGE
- CURRENT
- RESISTANCE

It was called

**OHM's LAW**






OHM's law formula:

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$

A little help...

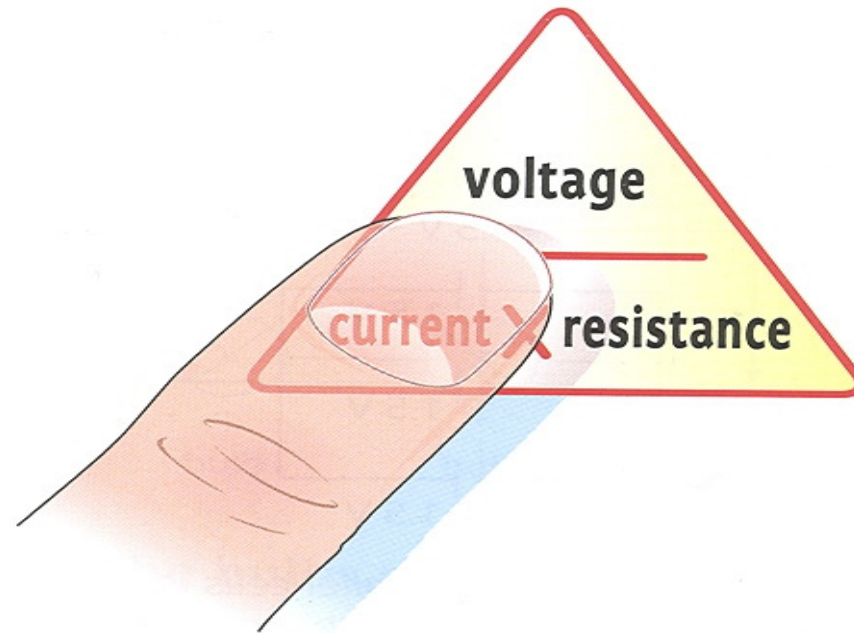

Look at these pictures...



Copyright © CCWB, LLC • ChampCar.ws