

WHERE?



CLIL

Project

HOW?




WHY?



WHAT?



Belén Gallego Sanz

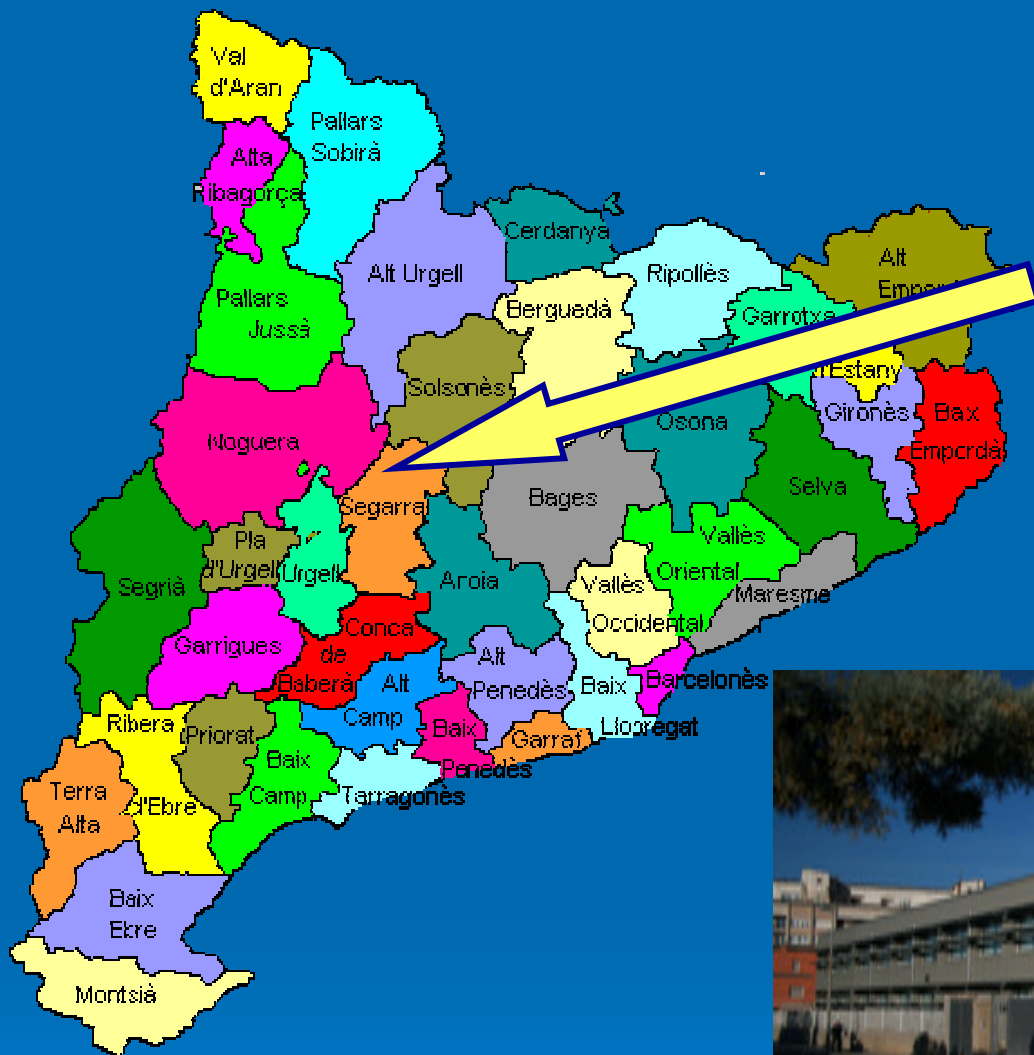

IES La Segarra

Background

- At the beginning it gave only courses of Vocational Education
- LOGSE: it became a Compulsory Secondary School.
- Offers:
 - ESO
 - Batxillerat
 - CFGM
 - CFGS
- 400 students:
 - Nearly 270 in ESO
 - The rest between Batxillerat and Vocational Education




Foreign Languages Innovation Programme





Proposal	Action to develop	Courses	Groups	Time
1. Practical part of Technology	1.1 Technology Workshop / Software Instructions	2 nd ESO	All	1 h/weekly
2. Didactic Sequences of different Areas or Modules	2.1 Warming up & relaxing exercises in PE	3 rd & 4 th ESO	All	20 min/weekly
	2.2 Software of modules of ICT	1 st , 2 nd & 4 th ESO	All	-
	2.3 Latin texts translation and Latin culture aspects	1 st & 2 nd Batxillerat	Humanistic	25% of the subject
	2.4 Sequences & Functions	3 rd ESO	All	30 h / course
	2.5 Abstract in Treball de Recerca	1 st & 2 nd Batxillerat	All	-
	2.6 Technical vocabulary & the electromechanical instruction manual	5 & 6 modules	1 st & 2 nd of electromechanical & vehicles GFGM	30 h / course
	2.7 Telephonic calls & costumer service	1 module	Course of Administration GFGM	15 h / course




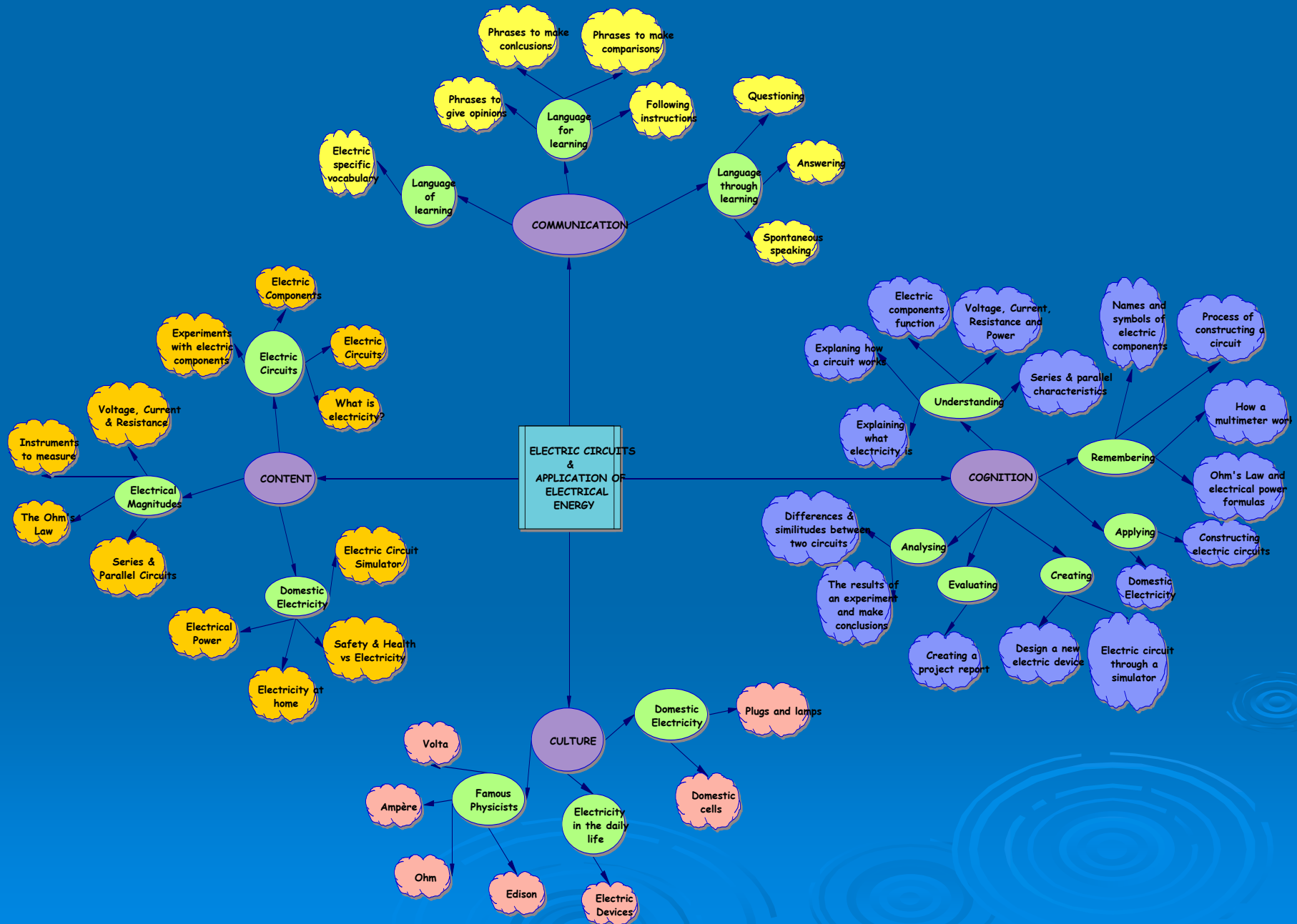
35 h module: Energy Production & Electrical Energy Application



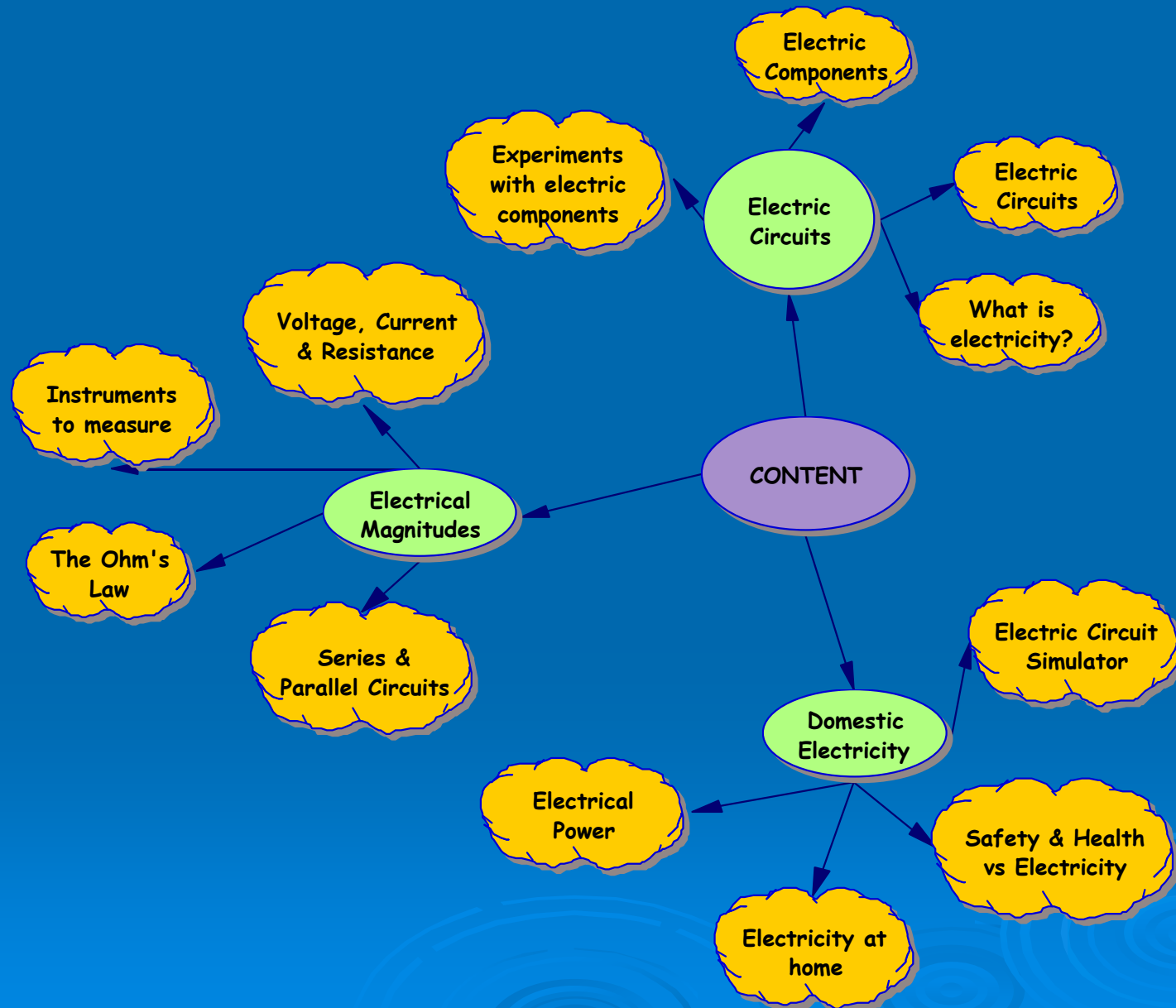

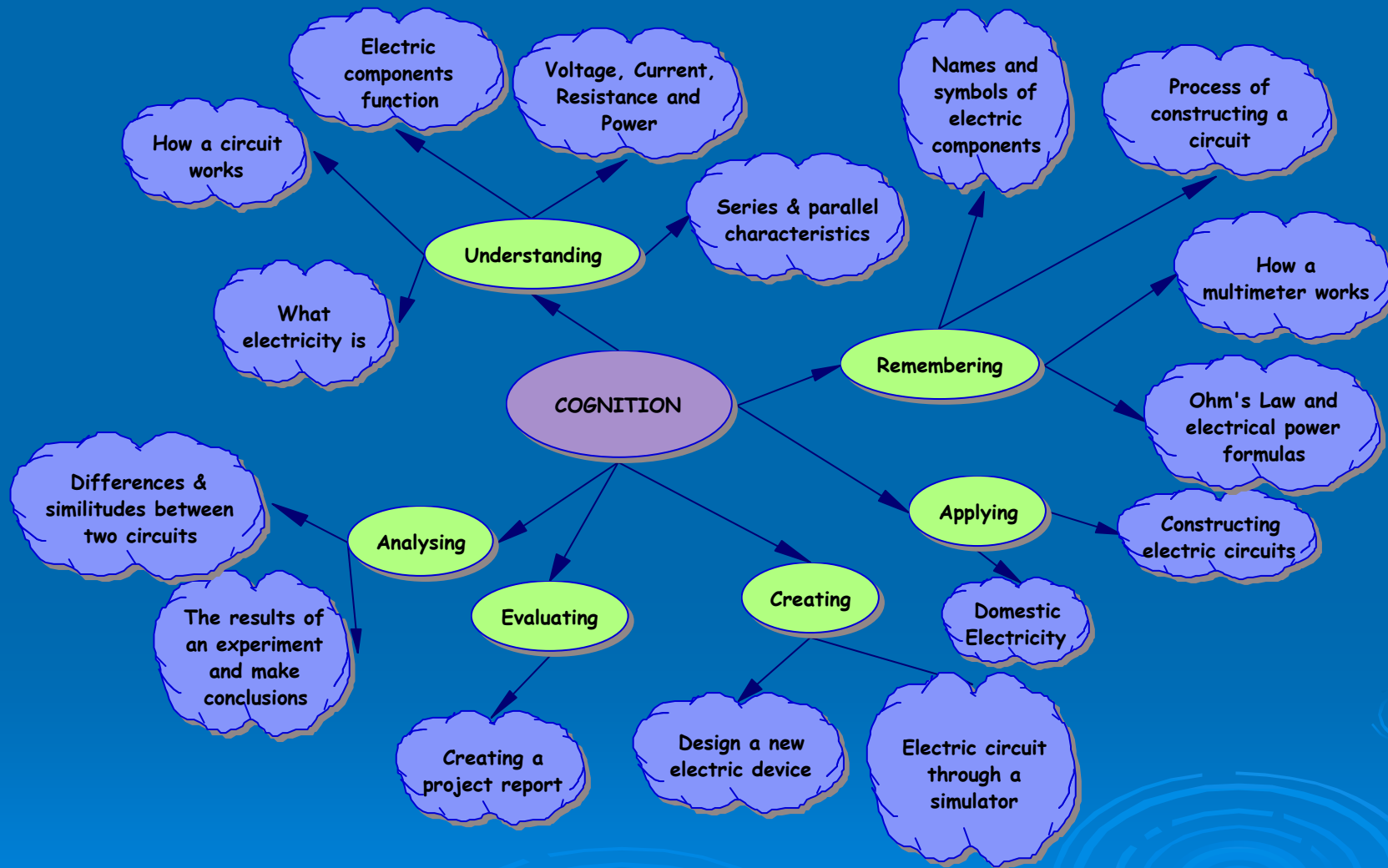

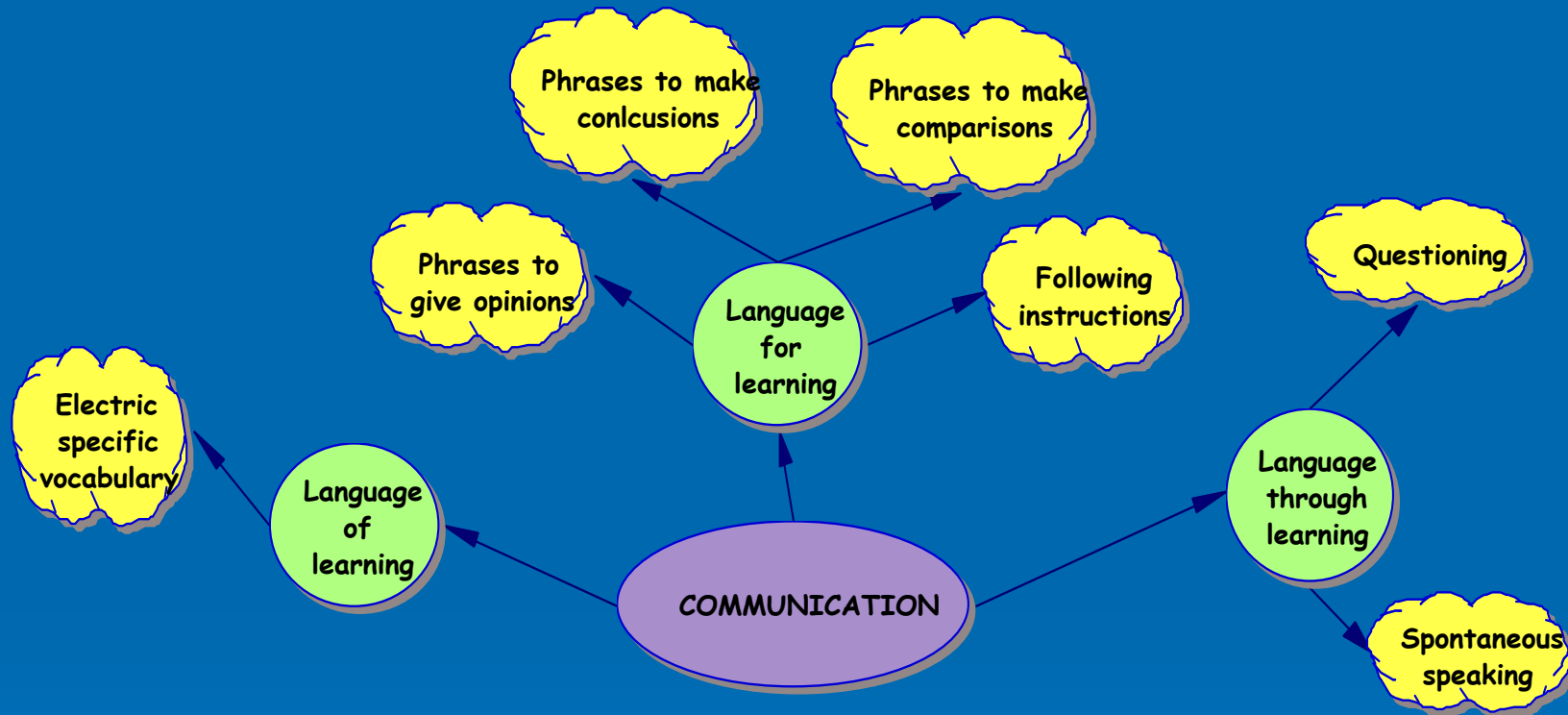

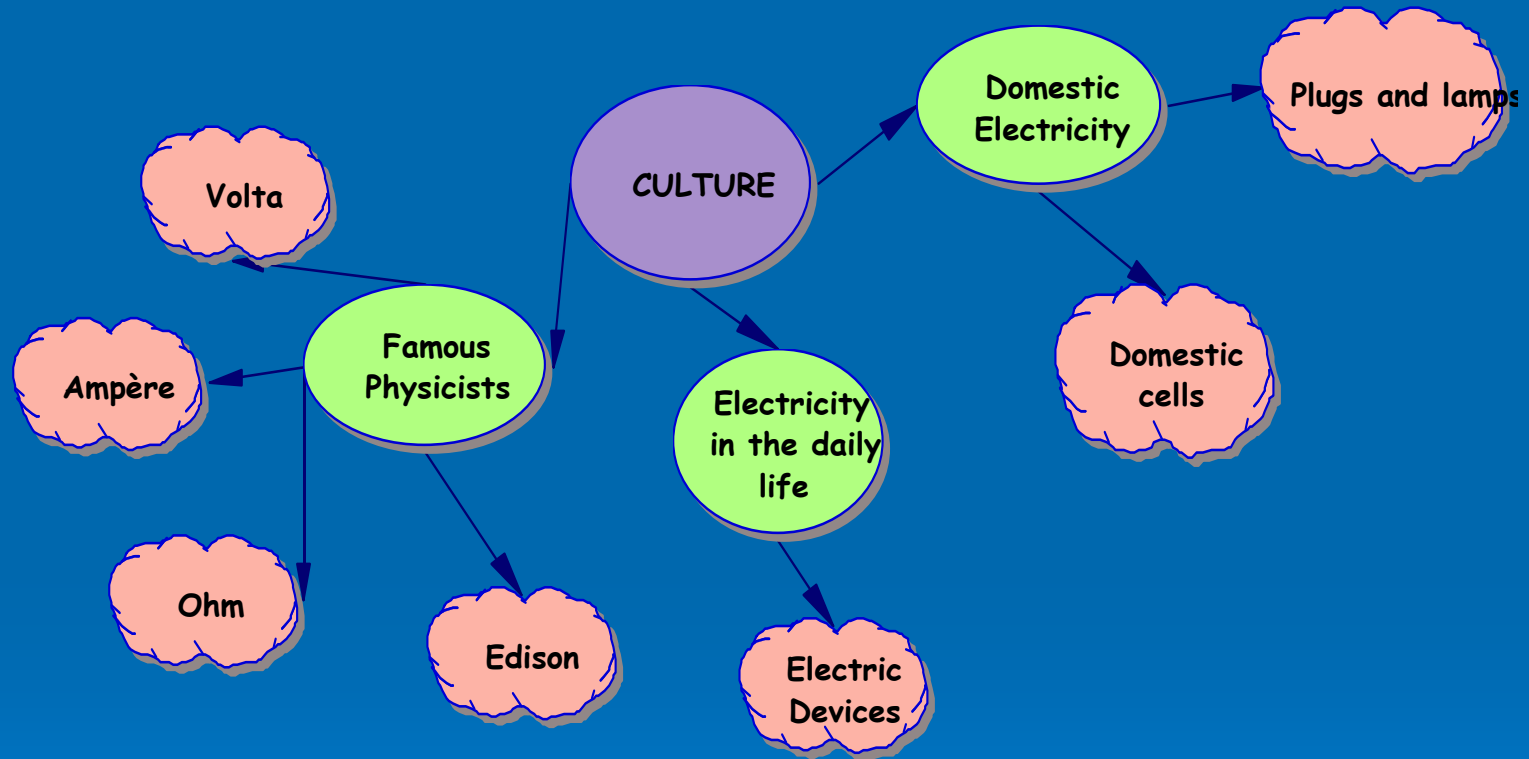

Materials

Technology Subject are divided in 2 parts:

- theoretical 1 h / weekly
- Practical 1 h / weekly

Example 1

Example 2


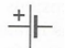

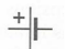

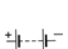


Example 3

Assessment











Theoretical: Lesson 3



GENERATORS

DC				
Picture	Name	Symbol	Energy transformation	Characteristics
	Cell		Chemical-Electrical	Non-rechargeable
	Accumulator		Chemical-Electrical	Rechargeable
	Battery		Chemical-Electrical	Group of accumulators. Rechargeable.
	Dynamo		Mechanical-Electrical	-


RECEIVERS

Picture	Name	Symbol	Energy transformation
	Bulb		Electrical- Light
	Buzzer		Electrical-Sound
	Bell		Electrical-Sound
	Engine	 Depends on the current	Electrical-Mechanical




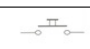


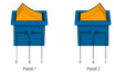

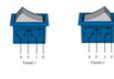
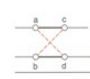
CONDUCTORS

Picture	Name	Symbol
	Cables/Wires	

Conductor: copper Insulator: plastic



CONTROLLERS

Picture	Name	Symbol	Characteristics
	Switch		1 entry-1 exit
	Push switch NO		1 entry-1 exit
	Push switch NC		
	Two-way switch		1 entry-2 exits
	Double pole switch		2 entries-2 exits


✚ Complete the chart below.

Electric Component	Name	Symbol	Energy Transformation
Generator	Accumulator		
			DC: Mechanical-Electrical
			AC: Mechanical-Electrical
			Electrical- Sound
	Bulb		
	Engine		

✚ Match the names with the right symbol.

Battery	
Push switch NC	
Two-way switch	
Double pole switch	
Accumulator	
Push switch NO	

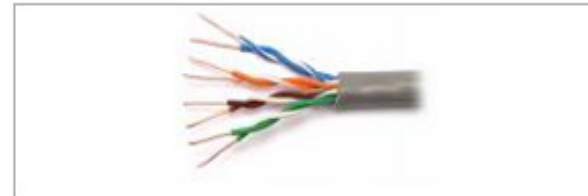✚ Put the names of the components of this wire:



Practical: Lesson 4

Electric Circuits

Experiments with Electric Components


DOING EXPERIMENTS

EXPERIMENT 1

Material:


- 1 battery 1.5 V
- 2 wires
- 1 buzzer
- push switch


Picture

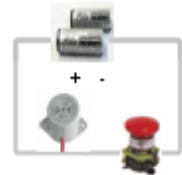

What's happened?

Underline the most suitable word in these sentences:

When the push switch is in OFF position  the circuit is open/closed. Electricity flows/does not flow.

When the push switch is in ON position  the circuit is open/closed. Electricity flows/does not flow.

When the push switch is in OFF position the buzzer rings/does not ring.

When the push switch is in ON position the buzzer rings/does not ring.

Circuit Diagram

Draw the diagram of the circuit.

Electric Circuits

Experiments with Electric Components

EXPERIMENT 2

Material:


- 1 cell 1.5 V
- 2 wires
- 1 buzzer
- 1 bulb 1.5 V
- 1 one-way switch

Picture



What's happened?

Complete these sentences:

When the one-way switch is in OFF  position the buzzer _____ and the bulb _____.

When the one-way switch is in ON position the buzzer _____ and the bulb _____.

Circuit Diagram

Draw the diagram of the circuit

Game...

In order to revise what we did last lesson we will play a game.

- You will have some filing cards (pictures, names or symbols).
- Everyone must complete one column (you must fix the filing card).
- One after another must ask another classmate for the filing cards they need to complete the column.
- The questions can be, for example:

Do you have the bulb picture?

☞

Do you have the bulb name?

☞

Do you have the bulb symbol?

- The answers can be:

No, I don't

☞


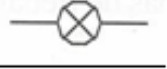
Yes, I do. Here it is!

☞

Yes, I do. Take it!

- Who completes their column first wins the game.

EXAMPLE:

Picture	Name	Symbol
	Bulb	



Practical: Lesson 8

Electrical Magnitudes

Introduction to series & parallel circuits

Game...

🎮 GAME: Instructions:

- ~~teacher~~ will give one of your classmates a piece of paper where a name of something related to electricity is written.
- the rest of the students will guess what it is
- you must ask questions until somebody guess the name

QUESTIONS you can use:

<p>1st questions:</p> <ul style="list-style-type: none">Is it an electric component?Is it an electrical magnitude?Is it an electrical magnitude's unit?Is it an electrical measuring device?
<p>2nd questions:</p> <p>For electric components:</p> <ul style="list-style-type: none">Does it give electrons energy?Is it an element that transforms electrical energy into another one?Does it transport electrons?Does it allow to complete or to break a circuit? <p>For electrical magnitudes:</p> <ul style="list-style-type: none">Is it the energy given to electrons to pass through a circuit?Is it the number of electrons every second?Is it the opposition to the passing of electrons? <p>For electrical magnitude's units:</p> <ul style="list-style-type: none">Is it the unit of voltage?Is it the unit of current?Is it the unit of resistance? <p>For electrical measure devices:</p> <ul style="list-style-type: none">Does it measure voltage?Does it measure current?Does it measure resistance?Does it measure all magnitudes?

DOING EXPERIMENTS

EXPERIMENT 1

FIRST PART

Material:

- 1 power source
- 2 multimeters
- 1 bulb 6V
- 1 one-way switch

Picture:

Instructions:

- Adjust the power source at 6V
- Put the **multimeter 1** in the voltage position as in the picture
- Select DC
- Select 30 V in the scale
- Put the **multimeter 2** in the current position as in the picture
- Select DC
- Select 20 A in the scale

Questions:

Volts multimeter 1	Volts power source	Amperes multimeter 2

Circuit Diagram

SECOND PART

Material:

- All components of the first part
- 1 bulb 6V

Picture:

Instructions:

- Adjust the power source at 12V
- Put the **multimeter 1** in the voltage position as in the picture
- Select DC
- Select 20 V in the scale
- Put the **multimeter 2** in the current position as in the picture
- Select DC
- Select 20 A in the scale

Questions:

Volts multimeter 1 for every bulb	Volts power source	Amperes multimeter 2
Bulb 1:		
Bulb 2:		

- Is the mark of the **multimeter 1** the double ($\times 2$) or the half ($\div 2$) of the mark of the power source?
- What happens when you adjust the power source at 6V? Underline the most suitable option:
Bulbs have more/less light

Circuit Diagram

THIRD PART

Material:

- All components of the second part
- 1 bulb 6V

Picture:

Instructions:

- Adjust the power source at 18V
- Put the **multimeter 1** in the voltage position as in the picture
- Select DC
- Select 20 V in the scale
- Put the **multimeter 2** in the current position as in the picture
- Select DC
- Select 20 A in the scale

Questions:

Volts multimeter 1 for every bulb	Volts power source	Amperes multimeter 2
Bulb 1:		
Bulb 2:		
Bulb 3:		

- Is the mark of the **multimeter 1** the triple ($\times 3$) or the third part ($\div 3$) of the mark of the power source?
- What happens when you increase one of the bulbs?
 - All bulbs do not light up
 - All bulbs light up
 - multimeter 2** marks 0.25 A
 - multimeter 2** marks 0 A

Circuit Diagram

Theoretical: Lesson 9

Electrical Magnitudes

Series & Parallel Circuits

CONNECTIONS OF CIRCUITS

When you connect bulbs in this way



it is a

SERIES CIRCUIT



Characteristics

Remember the experiments you did in the workshop.

Work in groups. Choose the most suitable option:

- Current through a receiver is the same in every one
- Current through a receiver is half, third ... than voltage of every receiver
- The voltage crossing every receiver is the same as the voltage at the power source
- The voltage crossing every receiver is half, third ... than voltage of every receiver
- If a bulb is disconnected the other ones do not light up
- If a bulb is disconnected the other ones light up
- The total voltage of the circuit is the sum (+) of the voltage crossing every receiver
- The total voltage of the circuit is the same as the voltage crossing every receiver

Technology

Belén Gallago

Electrical Magnitudes

Series & Parallel Circuits

- The total current of the circuit is the sum of the current through every receiver
- The total current of the circuit is the same as the current through every receiver

Write correct sentences:

More things....

Batteries	CONTROLLERS
<p>The total voltage is the SUM of voltage of every cell. It is useful if we want to increase the TOTAL voltage of a circuit.</p>	<p>A circuit is complete when ALL controllers are in ON position.</p>

Technology

Belén Gallago



Theoretical: Lesson 7

Electrical Magnitudes

The Ohm's Law

Ohm's Law

In an electric circuit VOLTAGE, CURRENT and RESISTANCE are closely related with each other.

This relationship is known as OHM'S LAW:

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$



You need a new lamp for your bicycle so you buy one. The filament of the bulb has 4Ω resistance and it takes a current of $0,8 A$. The shop assistant did not give you a battery so now you must buy one. What voltage must battery have?

To resolve this problem it is helpful to use this triangle.



Resistance = 4Ω

Current = $0,8 A$

Voltage = ?

Answer

(you must cover with your finger the magnitude you are looking for. Operation: multiplication)

$$V = 0,8 A \times 4 \Omega \quad V = 3,2 \text{ volts (V)}$$

you must buy a $3,2$ v battery.

Tecnología

Belen Gallego

Electrical Magnitudes

The Ohm's Law

Some Exercises

1. What operation do you must do in every case?

If I do not know...

- the current I must _____ (multiply / divide) _____ (voltage / current / resistance) by _____ (voltage / current / resistance)
- the voltage I must _____ (multiply / divide) _____ (voltage / current / resistance) by _____ (voltage / current / resistance)
- the resistance I must _____ (multiply / divide) _____ (voltage / current / resistance) by _____ (voltage / current / resistance)

Now practise this new concept:

2. The circuit of a little torch  has 3Ω of resistance. It has inside a $4,8$ v battery. What is the current through the circuit?




Voltage =

Resistance =

Current =

Answer =

3. One of your friend has given you a lamp  that has 625Ω and the current flowing through it is $0,2 A$. What is the voltage?



Voltage =

Resistance =

Current =

Answer =

Tecnología

Belen Gallego

4. Your stereo player needs four 4.5 v cells to work and pass through the circuit a 2 A current. Do you know what the resistance of the circuit is?

	Voltage =
	Resistance =
	Current =
	Answer =

5. The battery of your mobile is 3.7 v and has a 5 Ω of resistance. What is the current through the battery if the switch is opened?

	Voltage =
	Resistance =
	Current =
	Answer =

6. Do you remember these pictures? Work in pairs.



- How can you increase the current (number of cars per minute) without modifying the engine of the cars? Choose the most suitable answer:

- making the road broader
- making the road narrower

So, in the case of an electric circuit we must:

- use a _____ (thicker/thinner) wire.
- _____ (increase/decrease) the resistance.

- How can you decrease the current without modifying the engine of the cars? Choose the most suitable answer:

- making the road broader
- making the road narrower

So, in the case of an electric circuit we must:

- use a _____ (thicker/thinner) wire.
- _____ (increase/decrease) the resistance.

- How can you increase the current without modifying size of the road?

- making an engine that gives more energy
- making an engine that gives less energy

So, in the case of an electric circuit we must:

- use a generator with _____ (more/less) voltage
- _____ (increase/decrease) the voltage.

- How can you decrease the current without modifying size of the road?

- making an engine that gives more energy
- making an engine that gives less energy

So, in the case of an electric circuit we must:

- use a generator with _____ (more/less) voltage
- _____ (increase/decrease) the voltage.

Write 4 conclusions:

If we want to	increase	the current, we must	increase	the voltage
	decrease		decrease	the resistance



Assessment

➤ Theoretical Lesson:

- Individual work
- Work in pairs
- What have I learnt?

In a plenary

➤ Practical Lesson:

- At the end of every unit students give the teacher the workshop worksheets

What have you learnt?

7. - Is it true? Is it false? Put a ✓

	True	False
Electrons are moving around the nucleus	<input type="checkbox"/>	<input type="checkbox"/>
Negatively charged atom has positive charge	<input type="checkbox"/>	<input type="checkbox"/>
Positively charged atom has more electrons than protons	<input type="checkbox"/>	<input type="checkbox"/>
Stable atoms have same number of electrons as protons	<input type="checkbox"/>	<input type="checkbox"/>
Atoms are made of molecules	<input type="checkbox"/>	<input type="checkbox"/>
Electrons move from positively charged material to positively charged material	<input type="checkbox"/>	<input type="checkbox"/>

Correct the false sentence. Write down the correction.

